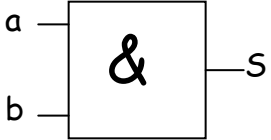
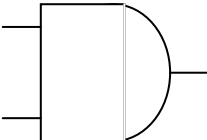
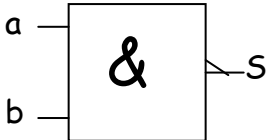
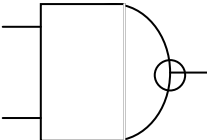


Les fonctions logiques



Fonction ET

Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = a \cdot b$	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>a</th> <th>b</th> <th>S</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	S	0	0	0	0	1	0	1	0	0	1	1	1
a	b			S														
0	0	0																
0	1	0																
1	0	0																
1	1	1																
																		



Fonction ET-NON

Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = \overline{a \cdot b}$	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>a</th> <th>b</th> <th>S</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	a	b	S	0	0	1	0	1	1	1	0	1	1	1	0
a	b			S														
0	0	1																
0	1	1																
1	0	1																
1	1	0																
																		

Fonction OU

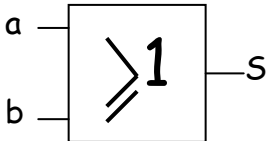
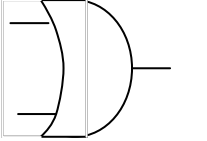
Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = a + b$	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>a</th> <th>b</th> <th>S</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	S	0	0	0	0	1	1	1	0	1	1	1	1
a	b			S														
0	0	0																
0	1	1																
1	0	1																
1	1	1																
																		

Fonction OU-NON

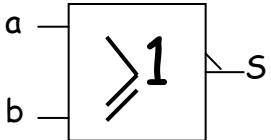
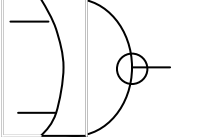
Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = \overline{a + b}$	<table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>a</th> <th>b</th> <th>S</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	a	b	S	0	0	1	0	1	0	1	0	0	1	1	0
a	b			S														
0	0	1																
0	1	0																
1	0	0																
1	1	0																
																		

Les fonctions logiques



Fonction OU-EX

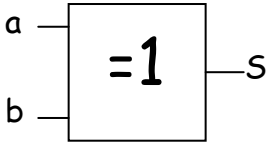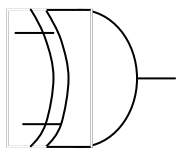Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = a \oplus b$	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th style="padding: 2px;">a</th> <th style="padding: 2px;">b</th> <th style="padding: 2px;">S</th> </tr> </thead> <tbody> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">0</td> <td style="padding: 2px;">0</td> </tr> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">1</td> <td style="padding: 2px;">1</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">0</td> <td style="padding: 2px;">1</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">1</td> <td style="padding: 2px;">0</td> </tr> </tbody> </table>	a	b	S	0	0	0	0	1	1	1	0	1	1	1	0
a	b			S														
0	0	0																
0	1	1																
1	0	1																
1	1	0																
																		

Fonction OU-NON-EX

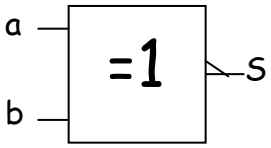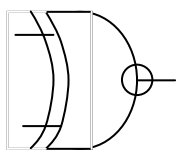Symbole électrique		On écrit	Table de vérité															
Europe	US	$S = \overline{a \oplus b}$	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th style="padding: 2px;">a</th> <th style="padding: 2px;">b</th> <th style="padding: 2px;">S</th> </tr> </thead> <tbody> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">0</td> <td style="padding: 2px;">1</td> </tr> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">1</td> <td style="padding: 2px;">0</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">0</td> <td style="padding: 2px;">0</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">1</td> <td style="padding: 2px;">1</td> </tr> </tbody> </table>	a	b	S	0	0	1	0	1	0	1	0	0	1	1	1
a	b			S														
0	0	1																
0	1	0																
1	0	0																
1	1	1																
																		

Fonction OUI

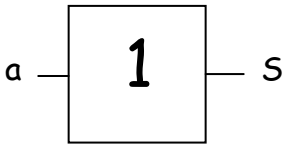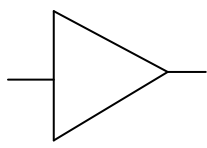Symbole électrique		On écrit	Table de vérité						
Europe	US	$S = a$	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th style="padding: 2px;">a</th> <th style="padding: 2px;">S</th> </tr> </thead> <tbody> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">0</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">1</td> </tr> </tbody> </table>	a	S	0	0	1	1
a	S								
0	0								
1	1								
									

Fonction NON

Symbole électrique		On écrit	Table de vérité						
Europe	US	$S = \overline{a}$	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th style="padding: 2px;">a</th> <th style="padding: 2px;">S</th> </tr> </thead> <tbody> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">1</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">0</td> </tr> </tbody> </table>	a	S	0	1	1	0
a	S								
0	1								
1	0								
